

## Unit 7: Semiconductor Diodes

Monday, 7 April 2025 12:10

Pure Silicon conducts electricity  
↳ But not very well

Silicon can be doped 2 ways  
↳ P-Type } Both conduct  
↳ N-Type } Better than pure silicon

Many types of Semiconductors  
↳ Silicon (Most common)  
↳ Germanium  
↳ Gallium-Based

P-Type (Has 'Holes')


↳ Doped with impurities such that it has an ABSENCE of electrons

N-Type (Has 'Extra')

↳ Doped with impurities such that it has EXTRA electrons
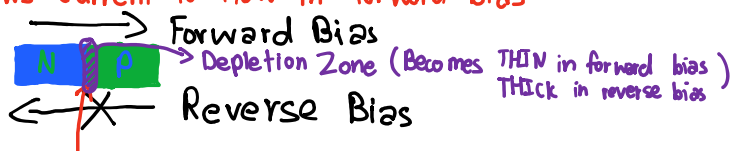
### Diodes



↳ Block current in reverse bias  
↳ Allows current to flow in forward bias



Junction is known as PN Junction

↳ Properties of Diodes

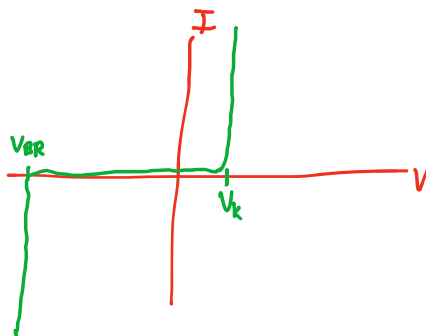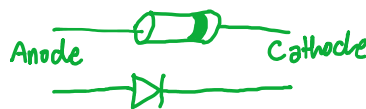- ↳ Diode Voltage ( $V_d$ )
  - ↳ Voltage across Diode
- ↳ Forward Voltage ( $V_F$ )
  - ↳ Voltage across Diode WHEN in Forward Bias!
- ↳ Knee Voltage ( $V_K$ )
  - ↳ Minimum Forward Voltage required to allow current to flow easily
- ↳ Breakdown Voltage ( $V_{BR}$ )
  - ↳ Reverse Voltage when an Avalanche Current will flow, in reverse Bias



### Ideal and Simplified Diode Model


↳ Practical Diode Model using Above Characteristic Graph

↳ Most Accurate

→ Ideal Diode Model uses simple Characteristic Graph

↳ Least Accurate

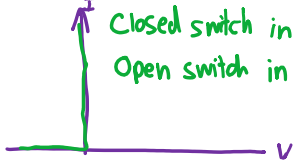
Closed switch in Forward Bias  
Open switch in Reverse Bias



→ Simplified Diode Model uses Simplified Characteristic Graph




↳  $\approx$  Accurate

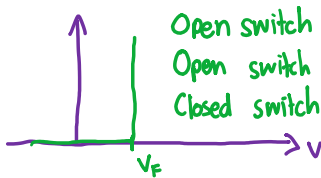Open switch in Reverse Bias  
Open switch in Forward Bias  $< V_k$   
Closed switch with voltage drop of  $V_F$  in Forward Bias  $\geq V_k$  (Like a Battery in Reverse Bias)





## Rectifiers


→ Half-Wave Rectifier

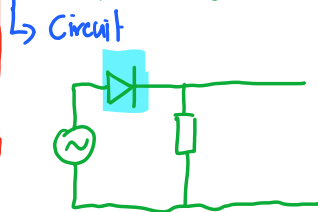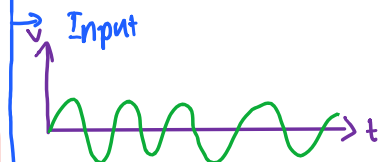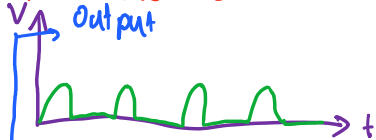



→ Full-Wave Rectifier

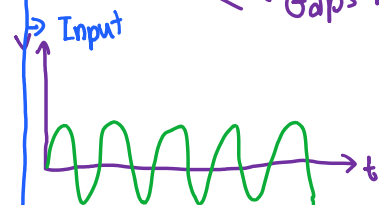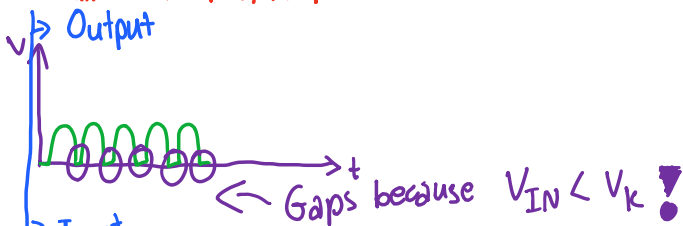

↳ Circuit

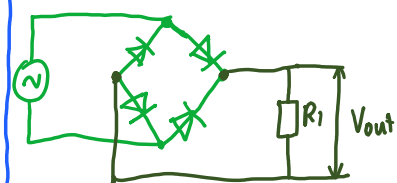

↳ Positive/Negative Cycle --- : Current

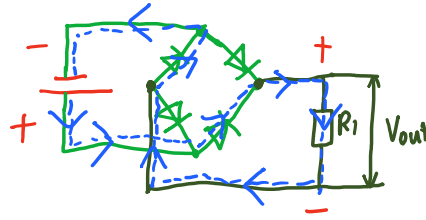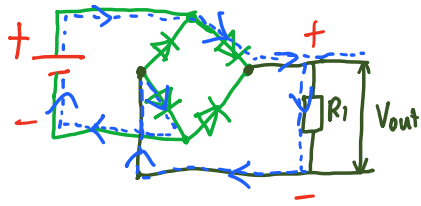


## Zener Diodes

- ↳ Replace breakdown voltage of normal diodes with Zener Voltage
- ↳ If  $V_{IN} \leq V_Z$ ,  $V_{out}$  is regulated at  $V_Z$
- ↳ Usually placed in Reverse Bias
- ↳ Acts like a normal diode in forward bias
  - ↳ Regulate at  $V_Z$  in Reverse Bias

Can be used with a rectifier & Voltage Smoothing Capacitor to regulate a smooth voltage (at  $V_Z$ )

## Darlington Pair

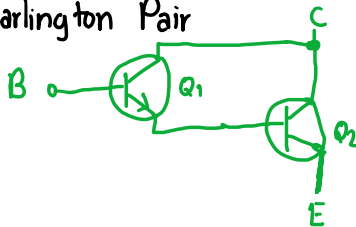

- ↳ If  $I_B$  is too small to get BJT into saturation region
  - ↳  $Q_1$  will amplify the signal for  $Q_2$  to work ( $\beta_1 \times \beta_2$ )
  - ↳ Use when Activation current is very small
- ↳ Only use when necessary (Disadvantages)
  - ↳ Slower switching speed
  - ↳ Need Higher Voltage (2 Base Activation Voltages required)
  - ↳ Higher voltage drop